

BRAC UNIVERSITY
Department of Electrical and Electronic Engineering
CSE350: Digital Electronics and Pulse Techniques

Experiment No: 1

Implementing Diode Logic (DL) gates

Objective:

1. Construction of DL gates.
2. Understanding the circuit operation

Circuit Diagram:

 


Fig 1: OR gate

 


Fig 2: AND gate

 


Fig 3: INVERTER for positive logic

Simulation tasks:

1. For DL OR and AND gate, assume the resistor value to be XXX where XXX is the last 3 digits of your student ID

1. Then draw the circuit as shown in Fig: 1,2 & 3 (In proteus)

2. Fill up the following table for OR gate, AND gate and inverter

V _A	V _B	V _{R1}	V _{R2}	I _{R1}	I _{R2}	V _R =Y

OR Gate

V _A	V _B	V _{R1}	V _{R2}	I _{R1}	I _{R2}	V _R =Y

AND Gate

V _i	V _{R1}	V _{R2}	V _{RC}	I ₁	I ₂	I _B	I _C	Y

Inverter

Report:

1. Explain the operation of diode AND circuit.
2. (For both circuits) Will the diodes D₁ and D₂ will work, if V_A=V_B=6V and V_R=5V?
(use Proteus to change input voltage levels and observe the output)
3. What is the function of R₂ = 100k at the base of an inverter in figure 3?
4. Verify that the transistor will be operating in the saturation and cutoff region in two cases for the inverter circuit (Use Proteus Data for verification)
5. Assuming OR gate , Draw the output

