

# CSE350

## Digital Electronics and Pulse Techniques

### Lab Report

#### Experiment No: 04

Analysis of the binary weighted and R/2R ladder D/A converters

#### Submitted by:

Name – Fariha Rahman

ID - 19101038

Section - 04

Department - CSE

Fall 2021

BRAC UNIVERSITY



## **Objective:**

The objective of this experiment is to construct two different D/A converter and to verify that digital signal is converted into proportional analog signal.

## **Equipment:**


Resistance = 10K, 20K, 5K, 2.5K, 1.25K

Dc source

Operational Amplifier


Multimeter

## **Circuit Diagram:**

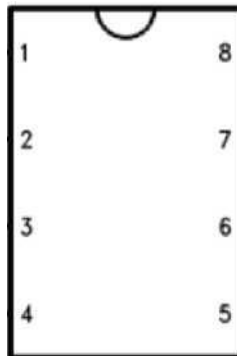



## Circuit Diagram 01
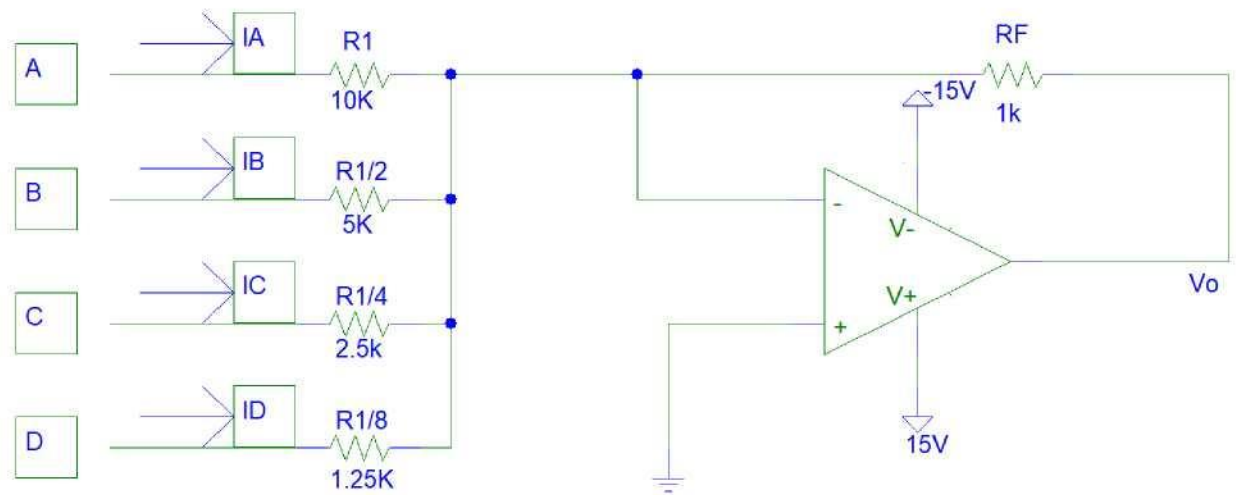
### Digital to Analog Converter using Binary-Weighted Resistors




## Circuit Diagram 02
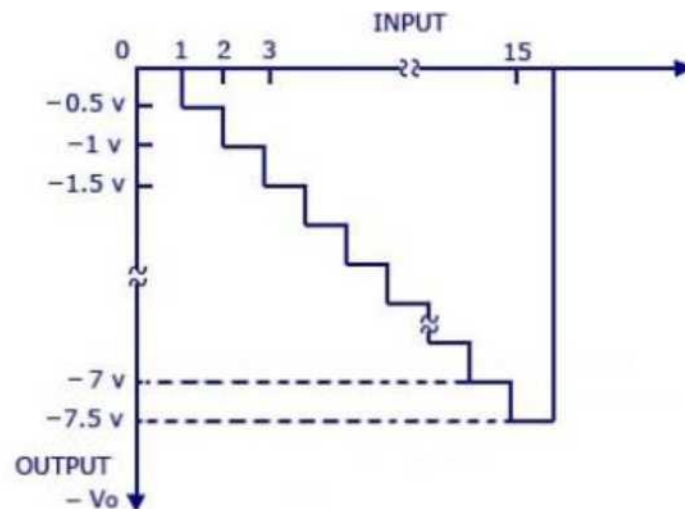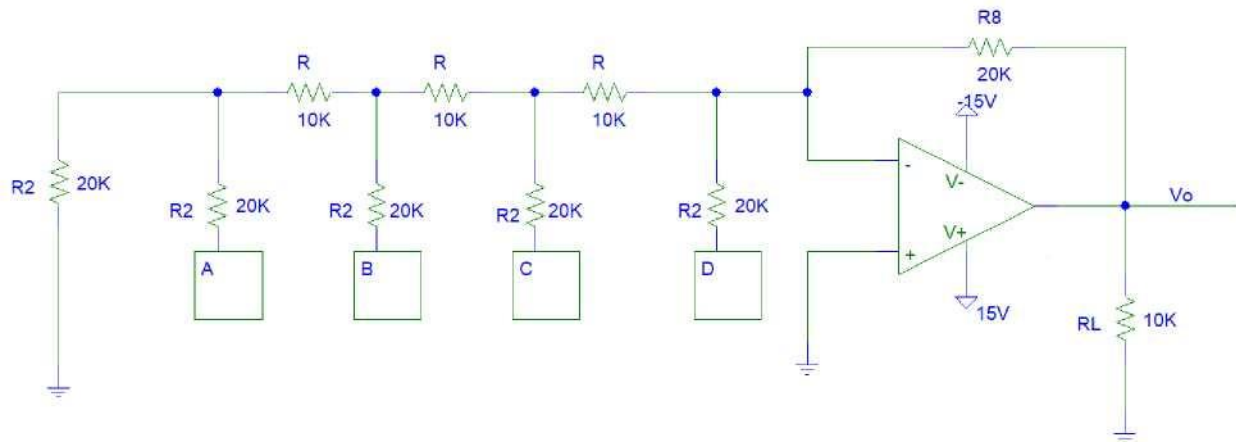
### Digital to Analog Converter with R and 2R Resistors




## Circuits:


## Circuit 01

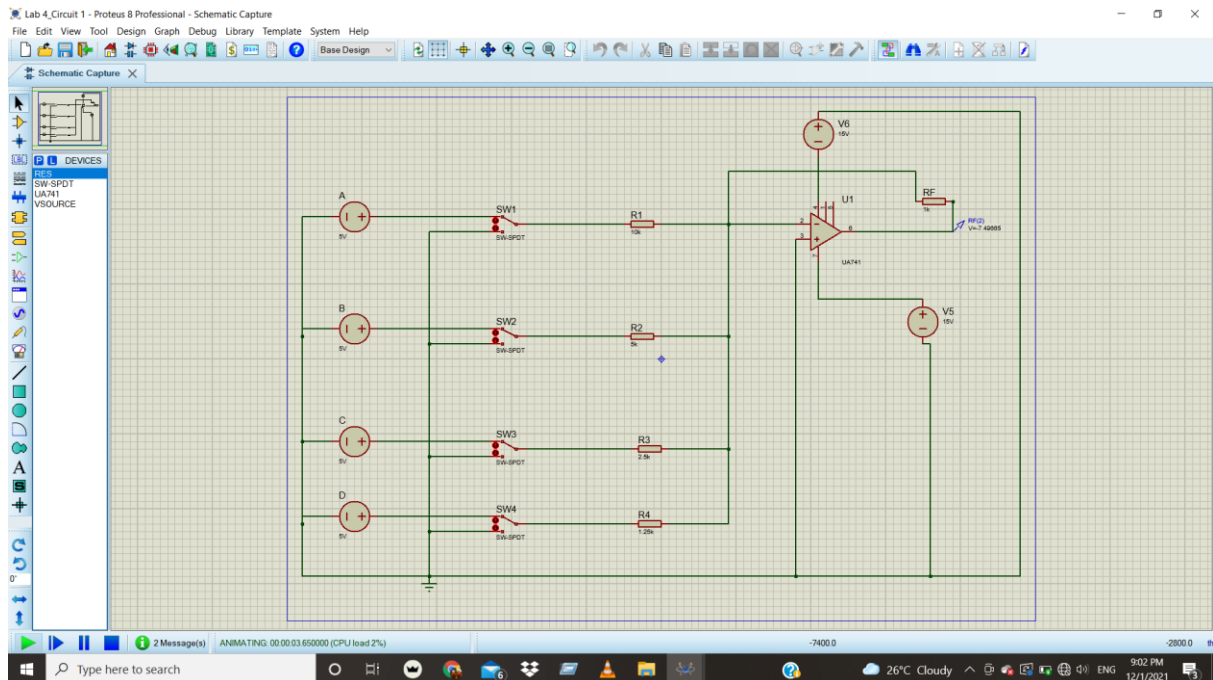


### Graph For Circuit 1:

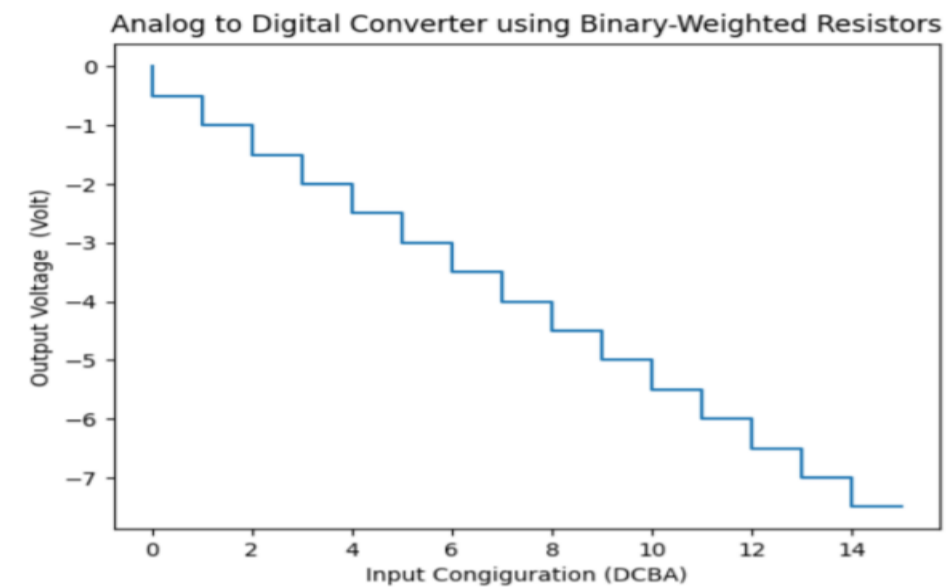

## Circuit 02

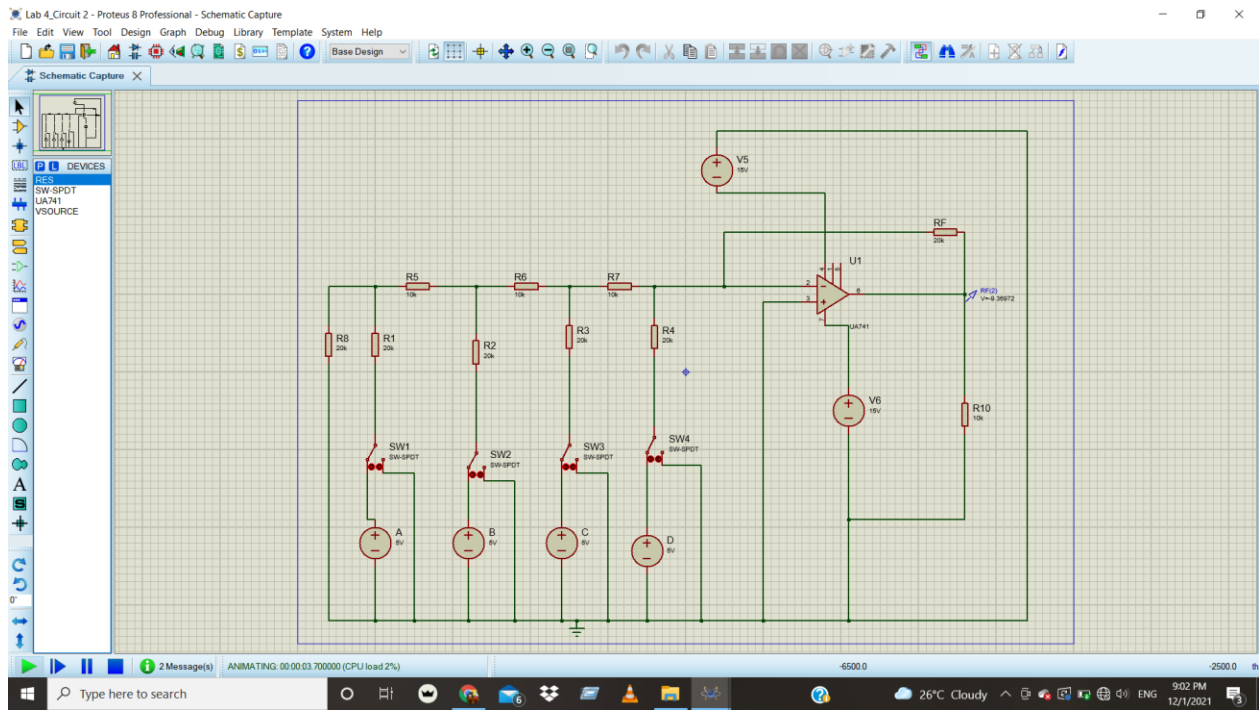

## Graph For Circuit 2:

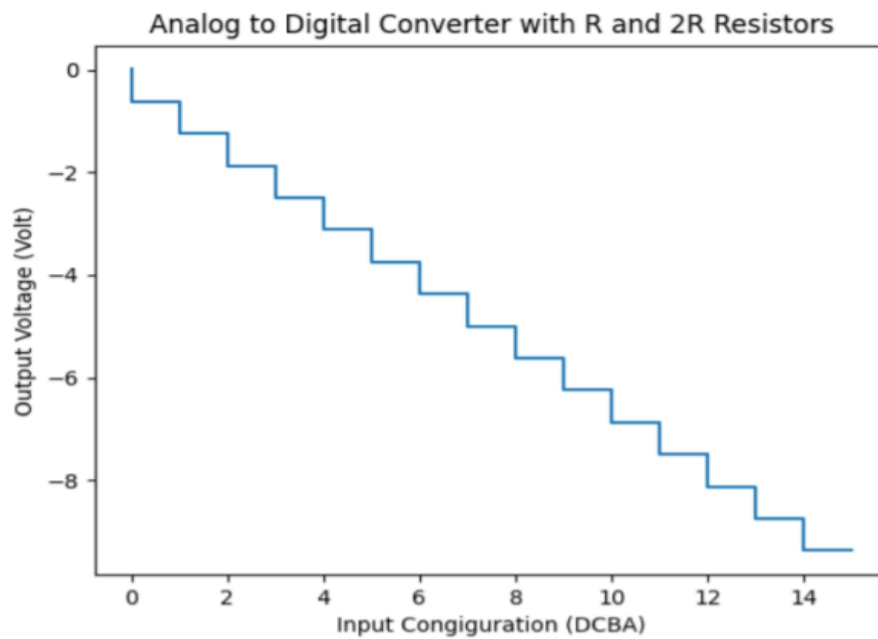

Data table: Circuit-1:

Input Configuration	D	C	B	A	Output Voltage, $V_o$ (V)
1	0	0	0	0	0.00272
2	0	0	0	1	-0.497259
3	0	0	1	0	-0.99723
4	0	0	1	1	-1.4972
5	0	1	0	0	-1.99714
6	0	1	0	1	-2.49712
7	0	1	1	0	-2.9971
8	0	1	1	1	-3.49708
9	1	0	0	0	-3.99685
10	1	0	0	1	-4.49683
11	1	0	1	0	-4.9968
12	1	0	1	1	-5.49678
13	1	1	0	0	-5.99672
14	1	1	0	1	-6.4967
15	1	1	1	0	-6.99667
16	1	1	1	1	-7.49665

Circuit-2

1	0	0	0	0	0.00495
2	0	0	0	1	-0.620026
3	0	0	1	0	-1.24501
4	0	0	1	1	-1.86999
5	0	1	0	0	-2.49496
6	0	1	0	1	-3.11994
7	0	1	1	0	-3.77992
8	0	1	1	1	-4.3699
9	1	0	0	0	-4.99487
10	1	0	0	1	-5.67985
11	1	0	1	0	-6.24983
12	1	0	1	1	-6.86981
13	1	1	0	0	-7.49478
14	1	1	0	1	-8.11976
15	1	1	1	0	-8.74479
16	1	1	1	1	-9.36972



Answer to the Question No-1 : By changing the value of  $R_F$  we can change the value of the step size. But there is only one condition and that is we need to set the step value in such a way that for any input our analog value must be less than (15 V), meaning output voltage should exceed saturation level of the opamp. So, it is not possible to get higher than 15 V in D/A converter.

Answer to the Question No-2 :

We know, Full step output = Reference voltage  $\times V_0$  (LSB)


For, Binary weighted D/A,  $\text{resolution value} = 1 - .4971 = .497$

$\therefore$  Full step output =  $15 \times .497 = 7.455 \text{ Volt}$


For, R and 2R R/A,  $\text{resolution value} = 1 - .6201 = .620$

$\therefore$  Full step output =  $15 \times .620 = 9.3 \text{ Volt}$







Answer to the Question No-3 :-






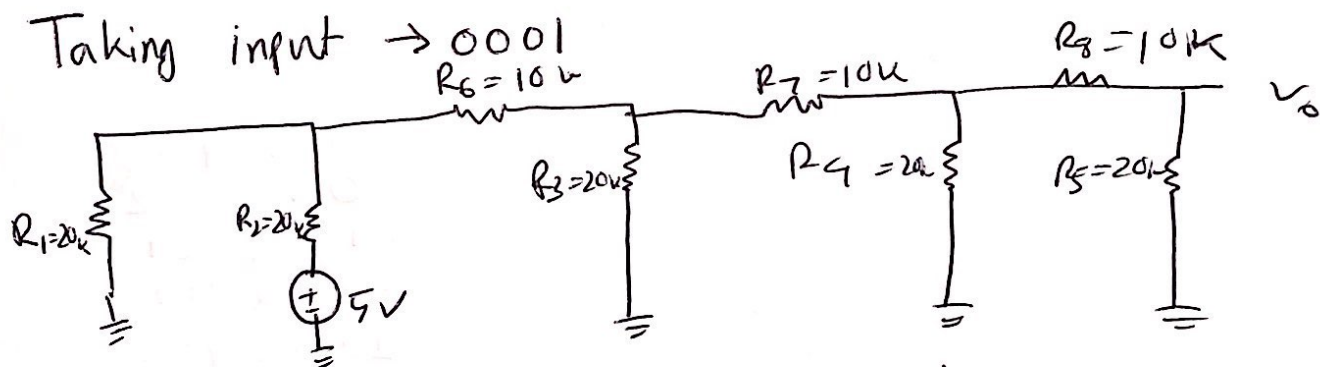


Now, Applying source transformation :

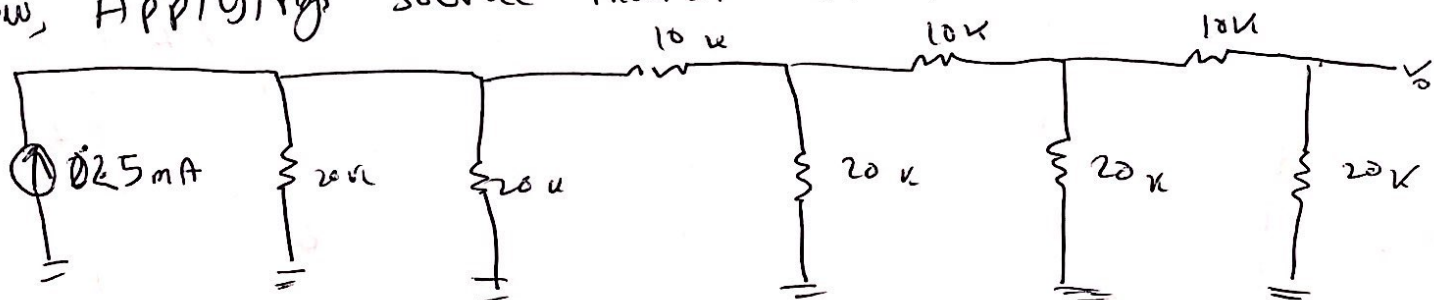



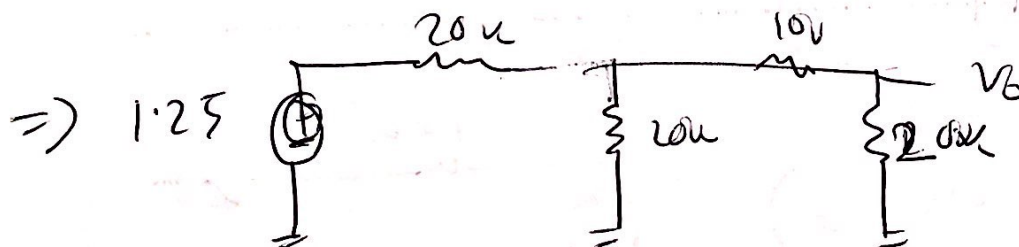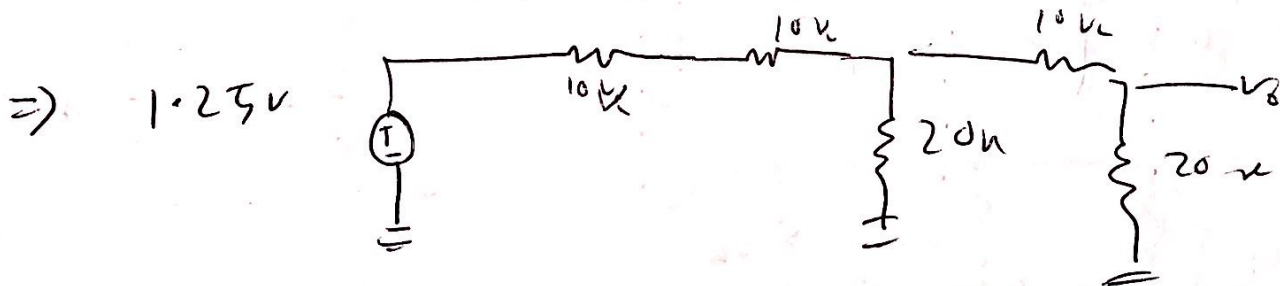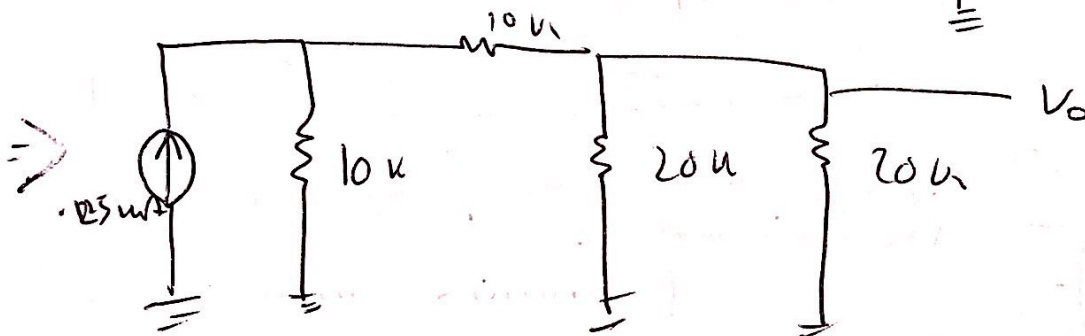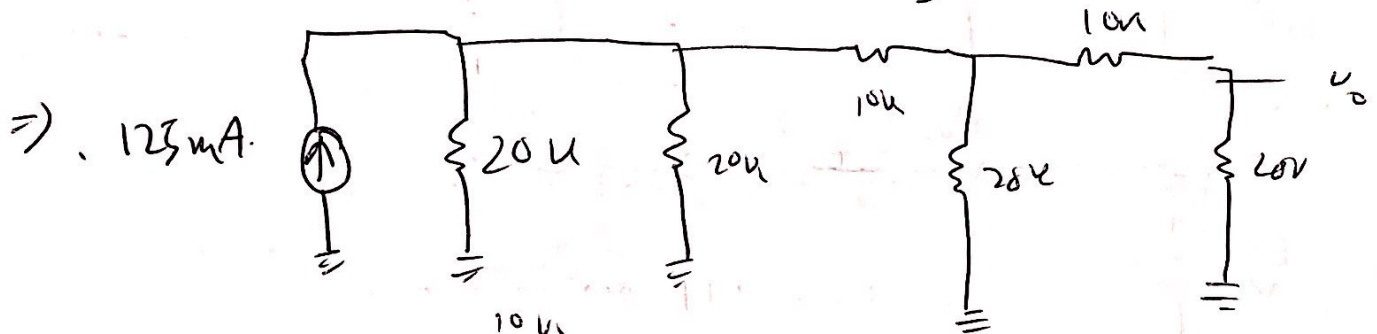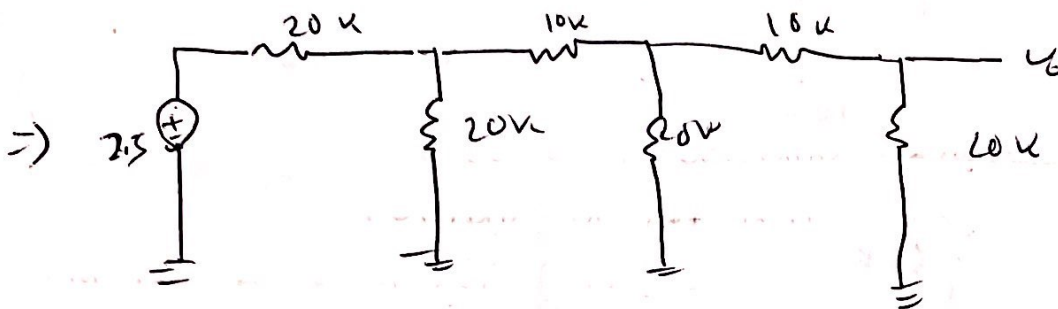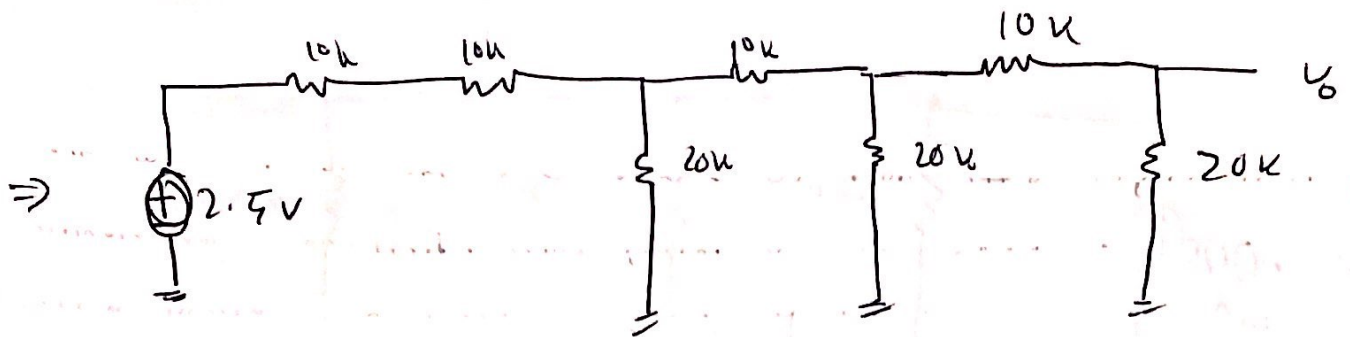

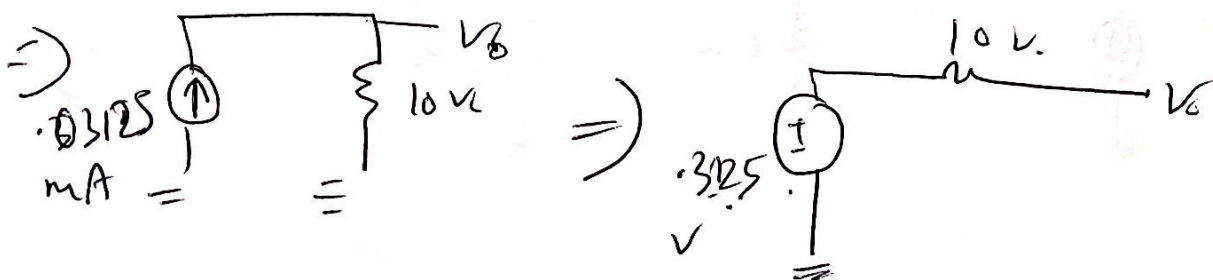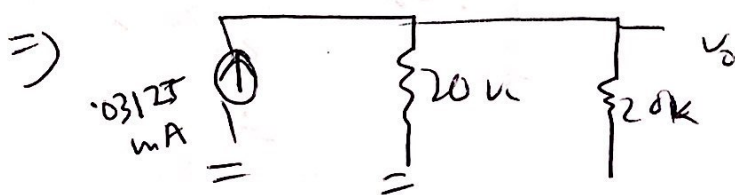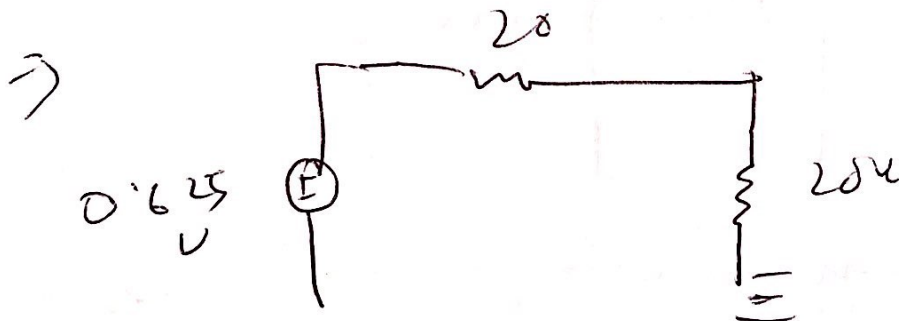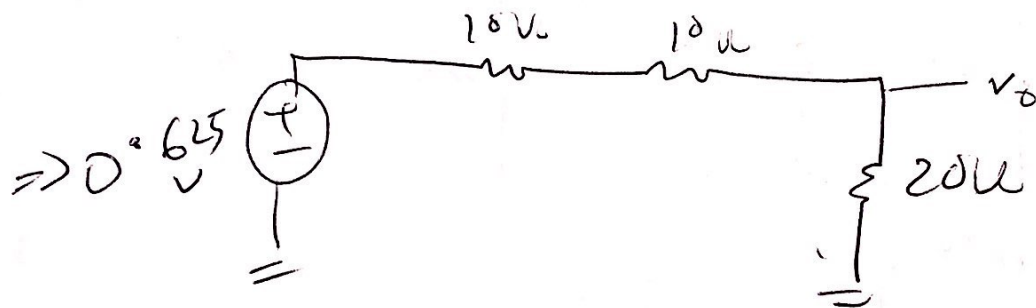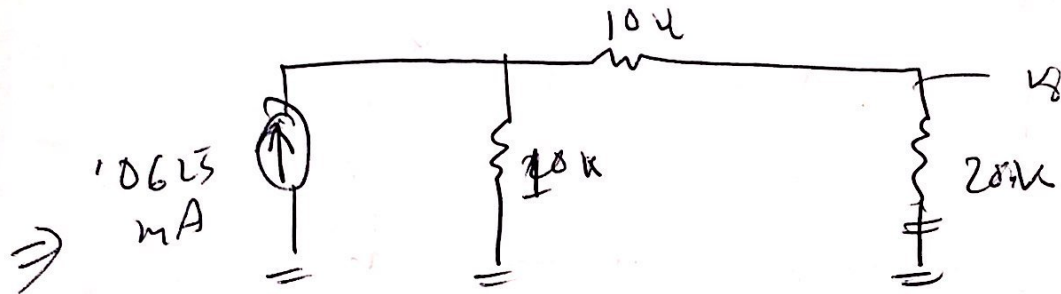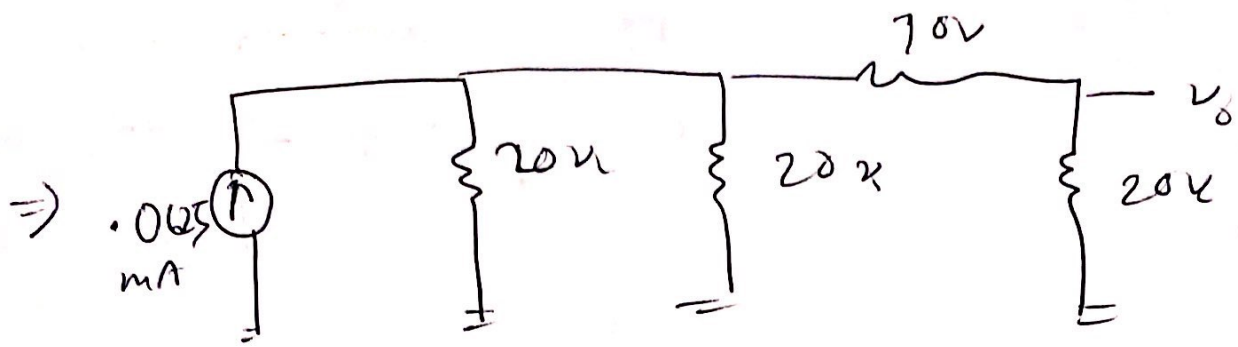

The closed loop voltage gain of an inverting amplifier is;

$$\frac{V_{out}}{V_{in}} = \frac{-R_f}{R_{in}}$$

$$\Rightarrow V_{out} = \frac{-20}{10} \times (0.3125) \\ = -0.625 \text{ V}$$

Answer to the Question No- 4 :

$$ID-19101038 \therefore V_A = V_B = V_C = V_D = 3 + 8 = 11 \text{ V}$$

Input Configuration	D	C	B	A	Output Voltage
1	0	0	0	0	0.0027228
2	0	0	0	1	-1.09729
3	0	0	1	0	-2.17717
4	0	0	1	1	-3.29713
5	0	1	0	0	-4.39698
6	0	1	0	1	-5.49694
7	0	1	1	0	-6.59688
8	0	1	1	1	-7.69684
9	1	0	0	0	-8.79639
10	1	0	0	1	-9.8963
11	1	0	1	0	-10.9962
12	1	0	1	1	-12.0962
13	1	1	0	0	-13.196
14	1	1	0	1	-13.4965
15	1	1	1	0	-13.4959
16	1	1	1	1	-13.4953



Answer to the Q. 5<sub>g</sub>

We know, Step size  $e = \left( \frac{R_F}{R_i} \right) V_{High}$

From this formula, it can be said that, by changing the value of  $R_F$ ,  $R_i$  and  $V_{High}$ , we can control the step size. It is seen that, the relationship between  $R_F$  and step size is proportional. That means If we increase  $R_F$ , the step size will increase too. and if we decrease the  $R_F$  and step size will decrease as well, but when the value of  $R_i$  and  $V_{High}$  is unchanged.