

# CSE 350

## Digital Electronics and Pulse Techniques

### Lab Report

#### Experiment No: 05

Analysis of triangular wave generator

#### Submitted by:

Name – Fariha Rahman

ID - 19101038

Section - 04

Department - CSE

Fall 2021

BRAC UNIVERSITY




## **Objective:**

The objective of this experiment is to analyze a bipolar and unipolar triangular wave generator.

## **Equipment:**


1. Trainer board
2. 741 op amp
3. Resistors: 10K (2 unit), 4K.
4. Capacitor: 0.05 or 0.4 $\mu$ F (1 unit)

## **Circuit Diagram:**

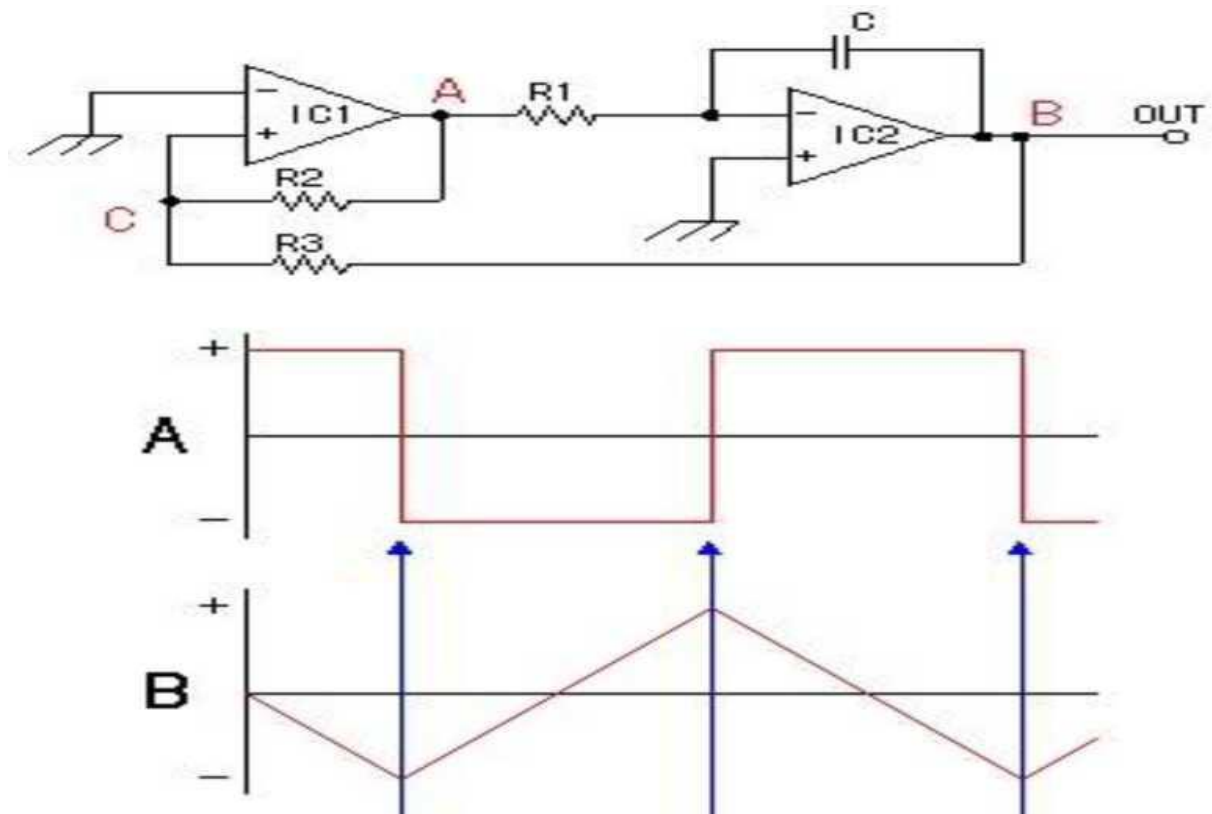


**Circuit:**

## Circuit 01

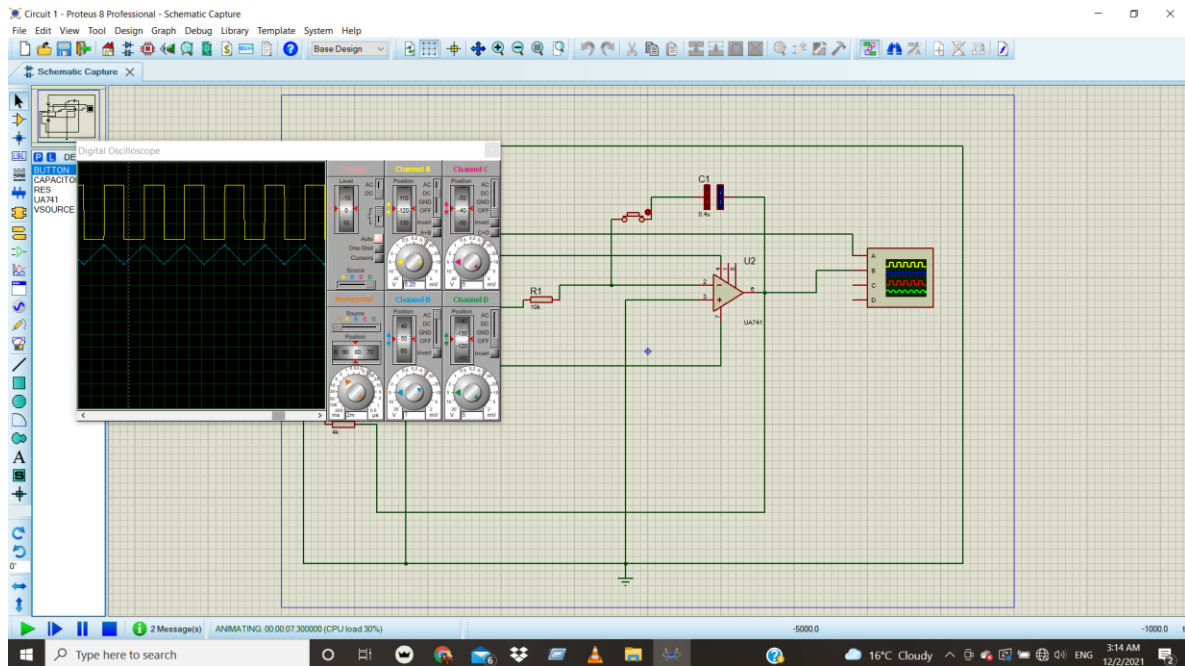

## Output

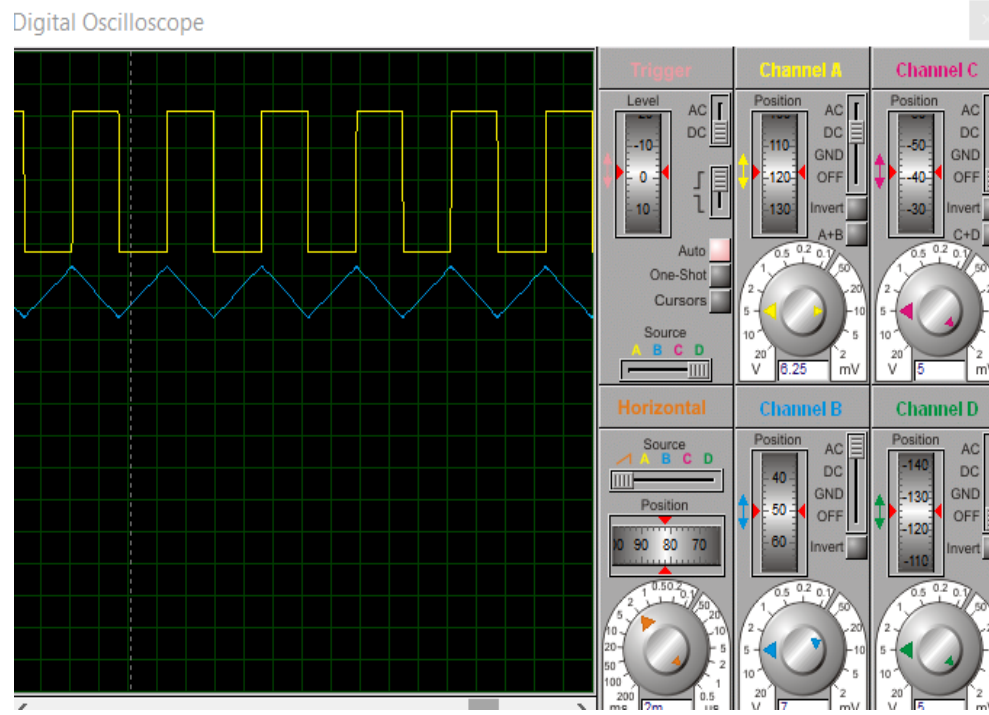

Data Table : Here, given,

$$R_1 = R_2 = 10 \text{ k}\Omega, \quad R_3 = 4 \text{ k}\Omega$$

$$C = 0.4 \mu\text{F}.$$

We know, Theoretical Frequency =  $\frac{1}{4 \times R_1 \times C} \times \frac{R_2}{R_3}$

$$\therefore f = \frac{1}{4 \times 10 \times 10^3 \times 4 \times 10^{-6}} \times \frac{10 \text{ k}}{4 \text{ k}}$$

$$= 156.25 \text{ Hz}$$

$\therefore$  Experimental Time Period,  $T = 12.9 - 6.4 \text{ ms}$   
 $= 6.5 \text{ ms}$

So, Experimental Frequency =  $\frac{1}{6.5 \times 10^{-3}} = 153.85 \text{ Hz}$

Theoretical Frequency $f$ (Hz)	Experimental Time Period, $T$ (ms)	Experimental Frequency $F$ (Hz)
156.25 Hz	6.5 ms	153.85 Hz

Report :

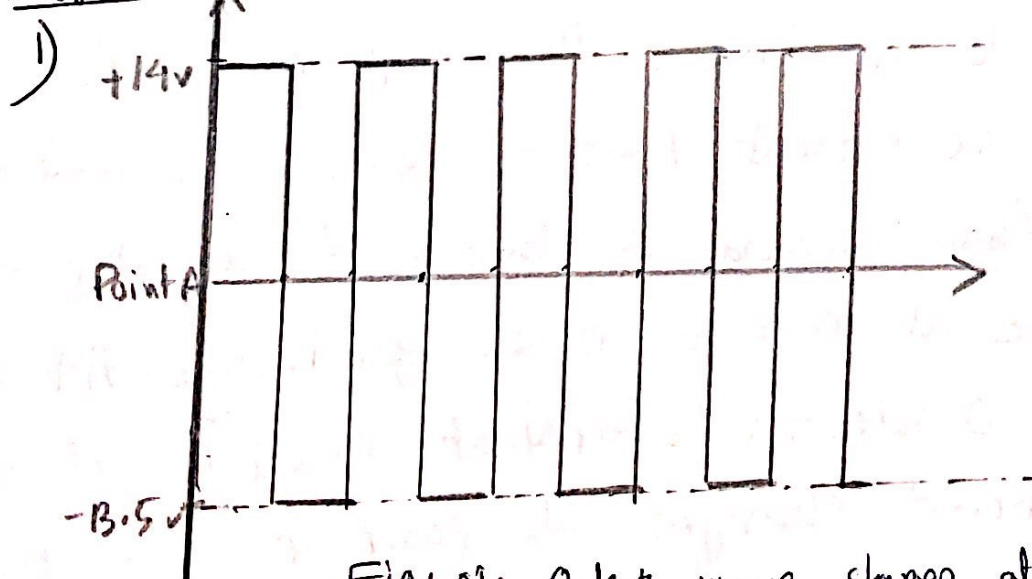


Fig. 01: Output wave shapes at Point A.

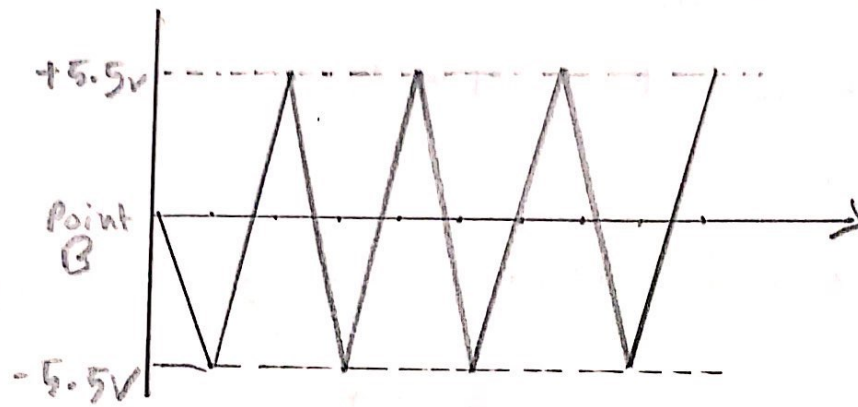


Fig 2: Output wave shape at point B.

### Answer to the Question No-2

In the circuit above,  $IC_1$  is the schmitt in circuit and  $IC_2$  is the integration circuit. Here, current flows from point A to B. through  $R_1$  resistor. Electric charge begins to store up at the left side of the capacitor C. Thus capacitor started increasing and that time, the output of  $IC_2$  at point B drops gradually. As B drops down, C also drops down. When voltage of C falls below 0, point A switches to negative. This happens for  $R_2 > R_3$  condition. So the current flow in reverse. In that time, current flows towards A through  $R_1$  resistor and the voltage at point B rises gradually. At point C exceeds 0 volts. the output of point A of the schmitt circuit changes to positive rapidly.



So, output of the integrator declines gradually and get a square output by point A and triangular wave from by point B.

Answer to the Q. No-3

No, the integrator circuit cannot be implemented with an inductor. If we use a inductor it will be a differential circuit.


Here,  $i_R + i_L = 0$

$$\Rightarrow \frac{V_s - 0}{R} + \frac{1}{L} \int_{-\infty}^t (V_o - 0) dt = 0$$

$$\Rightarrow \frac{V_s}{R} + \frac{1}{L} \int_{-\infty}^t V_o dt = 0$$

$$\Rightarrow \frac{d}{dt} \left[ \int_{-\infty}^t V_o dt \right] = -\frac{L}{R} V_s$$
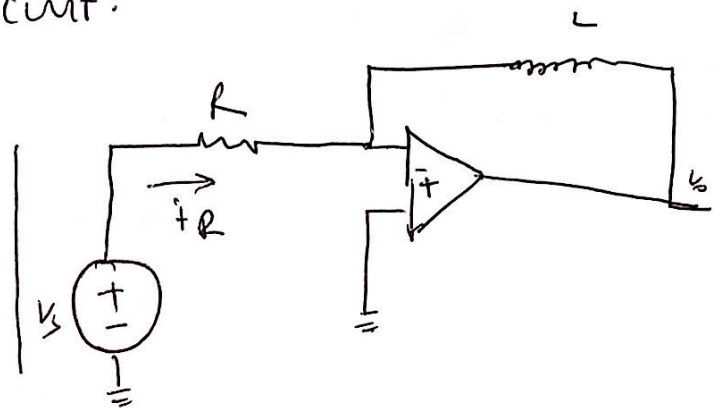
$$\Rightarrow V_o(t) = -\frac{L}{R} \frac{d}{dt} V_s$$



$$V = L \frac{di}{dt}$$

$$\therefore i = \frac{1}{L} \int V dt$$

So, we can say that, integrator circuit cannot be implemented with an inductor, as capacitor has wide range and more accurate than inductors.